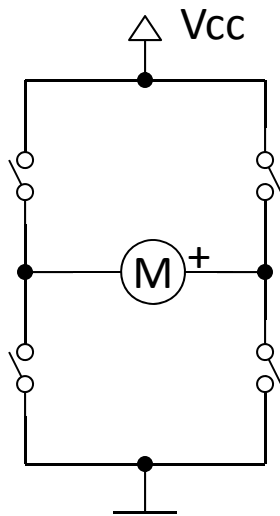



H-Bridges

H-Bridges


- Circuits that uses switches to reverse the direction of the current



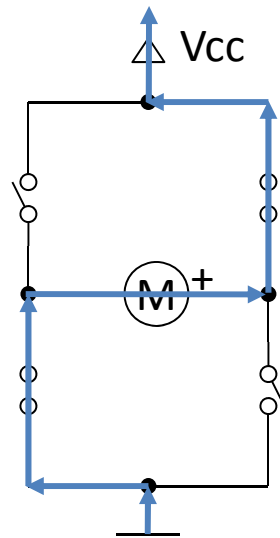
Circuit is open;
motor is free to
rotate in either
direction



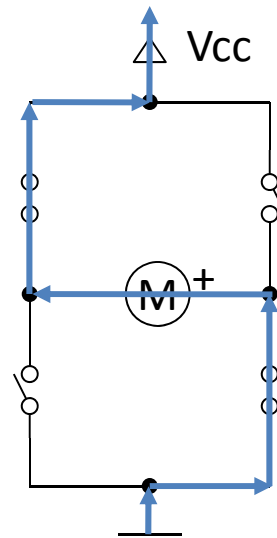Diagonal switches (top
right, bottom left)
are closed; motor spins in
positive (CCW)
direction



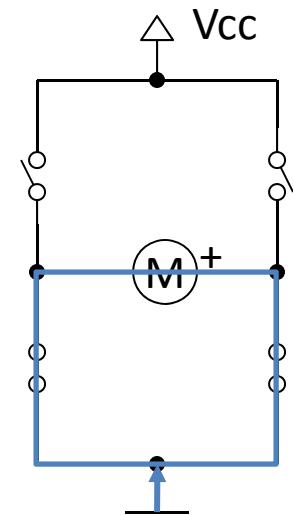Diagonal switches (top
left, bottom right)
are closed; motor spins in
negative (CW)
direction





Bottom switches
are closed; motor
terminals are
grounded, which
stops motor

Direction Control (Transistor H-Bridges)

Action	B3	B2	B1	B0
Free rotation	1	0	1	0
Forward	1	1	0	0
Backward	0	0	1	1
Brake	1	1	1	1

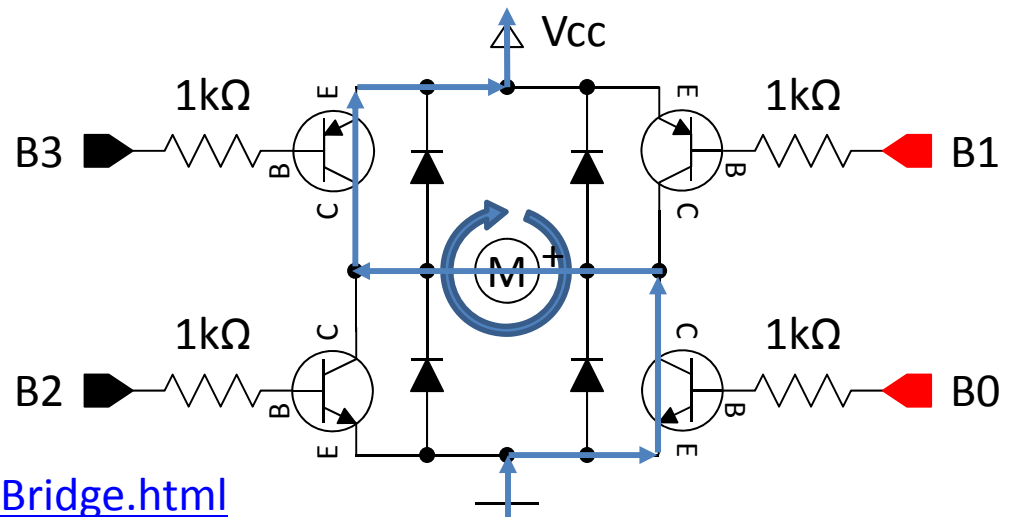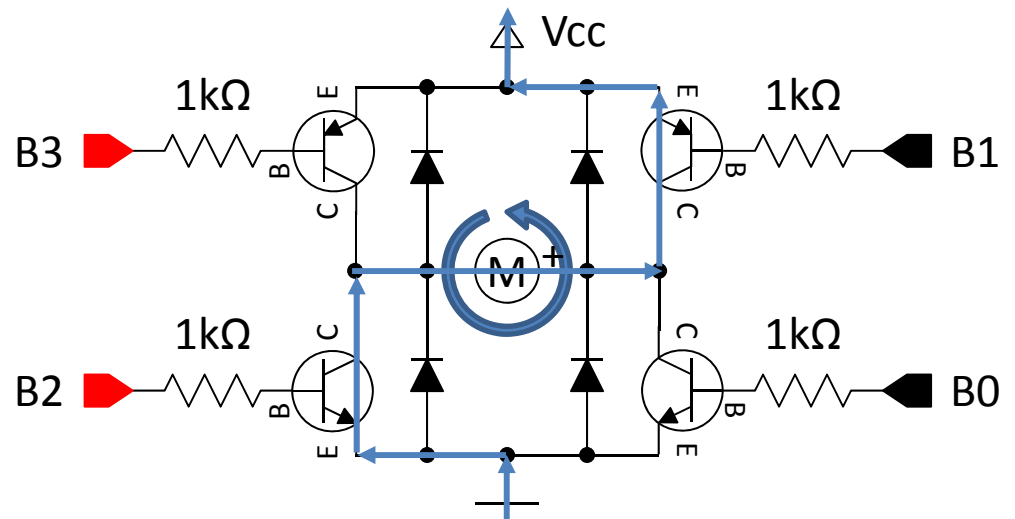Transistors act as electronic switches which can be controlled by the digital output of a microcontroller and can direct the flow of current in the circuit with little current applied to the base of each transistor





<http://www.robotroom.com/BipolarHBridge.html>

Lab


- Brushed DC Motor Control
 - Building and controlling a brushed DC motor using an H-bridge circuit and the NXT Sensor Expansion Kit

Transistor H-Bridge

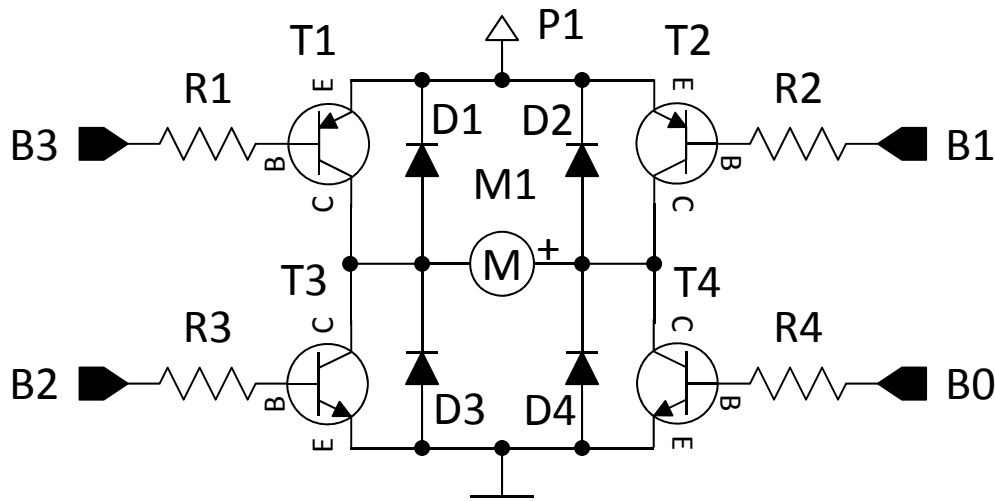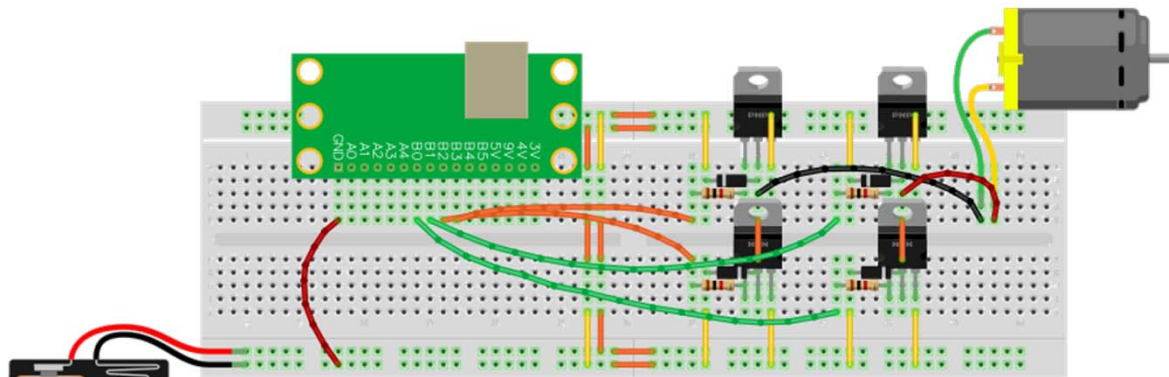


Part	Name	Value
Resistor	R1	1k Ω
	R2	1k Ω
	R3	1k Ω
	R4	1k Ω
Transistor	T1	PNP
	T2	PNP
	T3	NPN
	T4	NPN
Diode	D1	Power
	D2	Power
	D3	Power
	D4	Power
Motor	M1	Brushed
Battery	P1	9V

Lab Setup

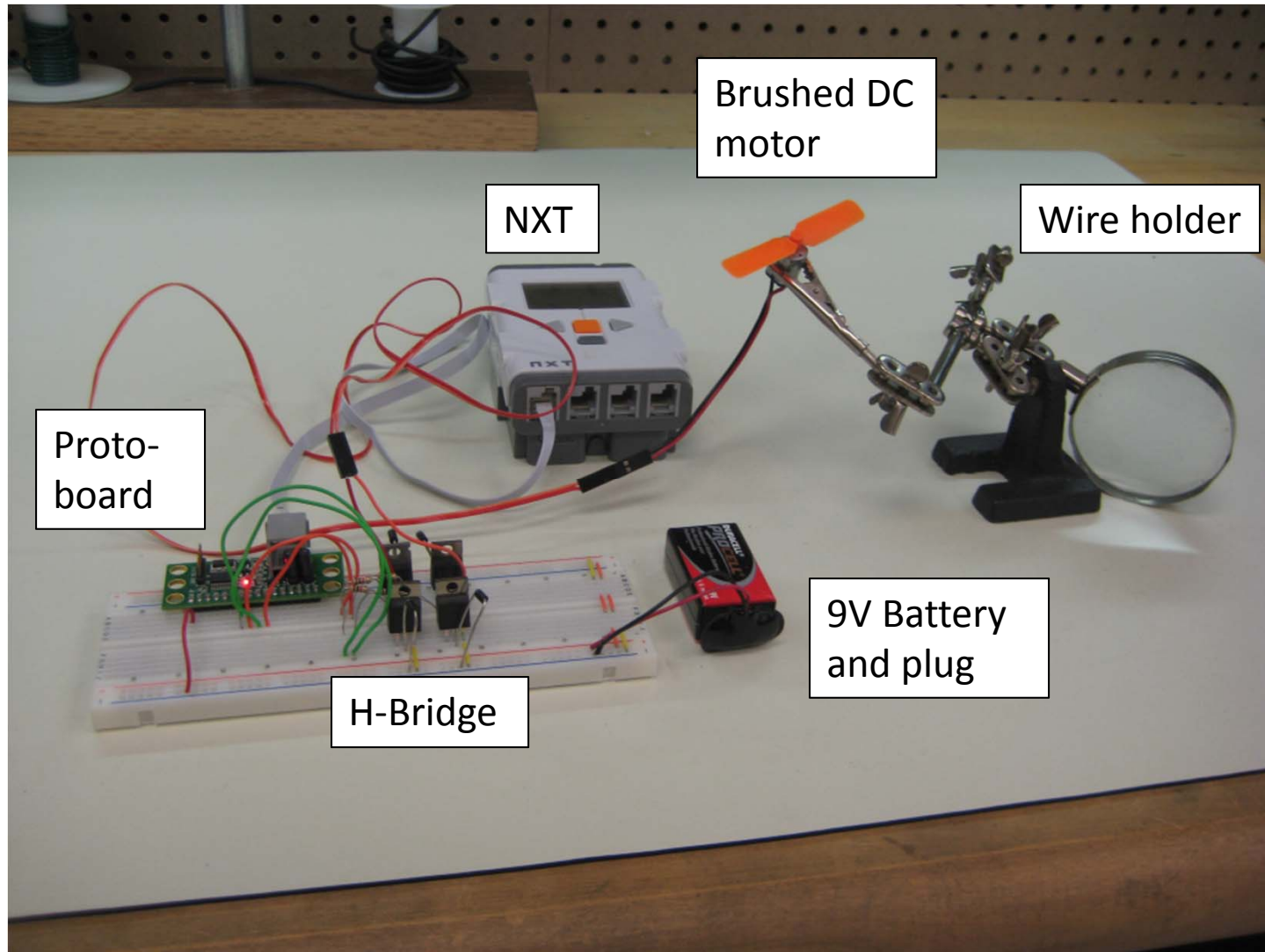

Circuit

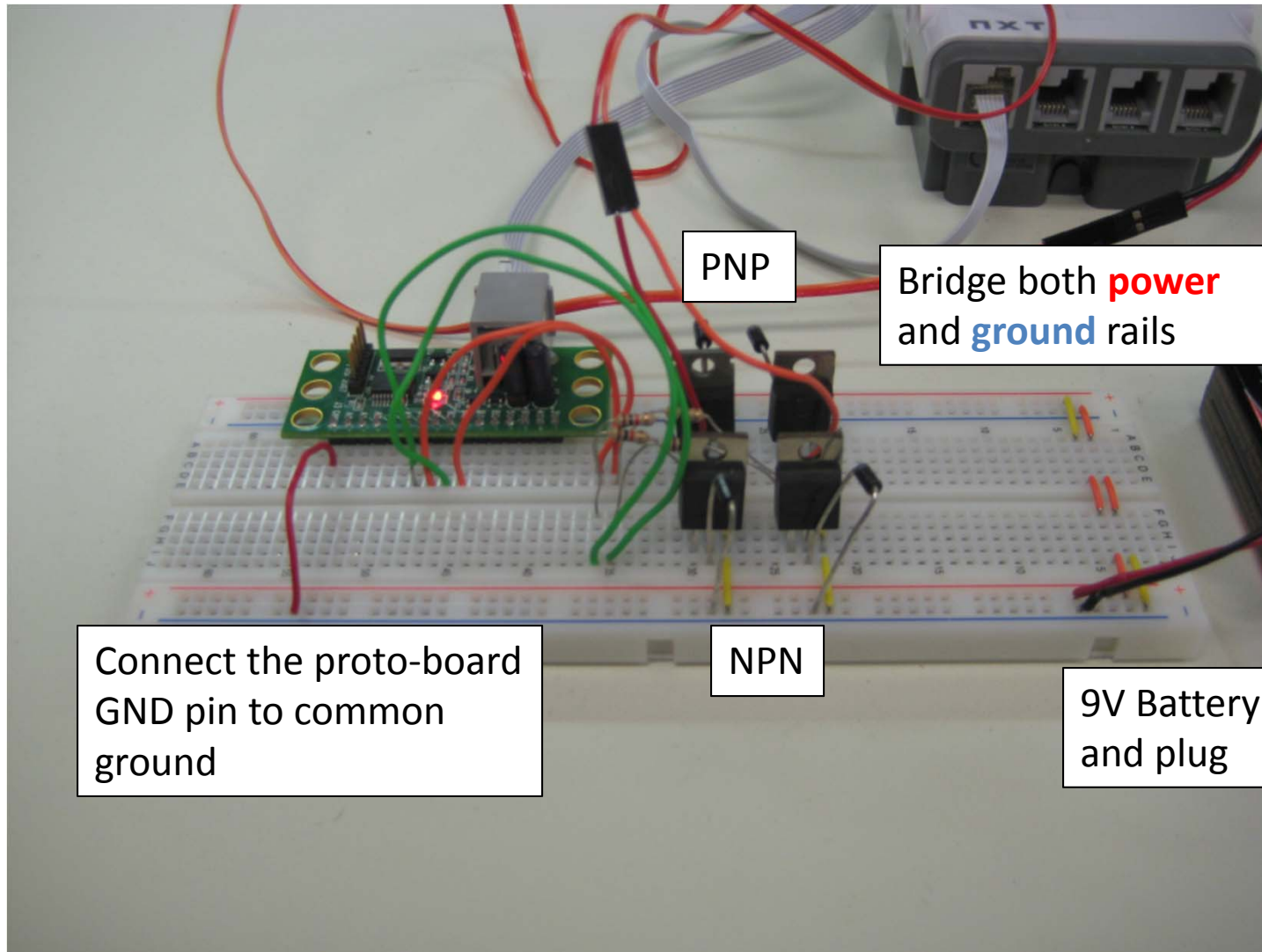

Output



Press the **center button** \square to let the motor spin freely

Press the **right button** $>$ to drive the motor backward



Press the **left button** $<$ to drive the motor forward

